

## Test 4

PH 112

Current and conductivity

Ohm's Law

Potential Field


Electrical energy and power

Combination of capacitors and resistors

KCL and KVL

RC circuits

### Example #1

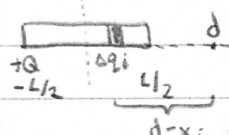


$$V_i = \frac{1}{4\pi\epsilon_0} \frac{\Delta q_i}{\Delta x_i} \quad \lambda = \frac{Q}{L} \quad dq = \lambda dx$$

$$V = \frac{1}{4\pi\epsilon_0} \int \frac{1}{d-x_i} dq = \frac{1}{4\pi\epsilon_0} \int_{-L/2}^{L/2} \frac{\lambda}{d-x_i} dx = \frac{1}{4\pi\epsilon_0} \frac{Q}{L} (-\ln(d-x)) \Big|_{-L/2}^{L/2}$$

$$= \frac{1}{4\pi\epsilon_0} \frac{Q}{L} (\ln(d+\frac{L}{2}) - \ln(d-\frac{L}{2}))$$

$$V = \boxed{\frac{Q}{4\pi\epsilon_0 L} \ln\left(\frac{d+L/2}{d-L/2}\right)}$$

### Example #2

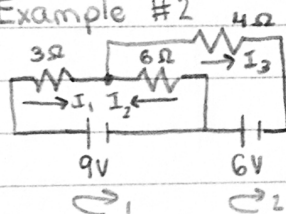

$$I_1 + I_2 = I_3 \quad \text{Loop 1: } \mathcal{E}_1 - I_1 R_1 + I_2 R_2 = 0$$

$$\text{Loop 2: } \mathcal{E}_2 - I_2 R_2 - I_3 R_3 = 0$$

$$9 - 3I_1 + 6I_2 = 0$$

$$6 - 6I_2 - 4I_3 = 0$$

$$I_1 = 2.33 \text{ A} \quad I_3 = 2 \text{ A}$$

$$I_2 = -0.33 \text{ A}$$